

# Lab 08

## Part A – Multiplexed 7-Segment Display

### Description

In this lab module, you learn about multiplexing applied to a 7-segment display to show multiple different values.

As usual, for this lab module, you will require a PC with a USB-A port to program the FPGA development board.

### Procedure

### Background

1. Listen to the description of the 7-segment display and its decoder's truth table. Some details are below.
  - The Basys 3 FPGA development board has a four-digit LED display, where each digit consists of seven segments (plus a dot, or decimal point).
    - You can find out more details about the seven-segment display specific to the Basys 3 board [here](#).
  - You may be familiar with this type of display from alarm clocks, microwave ovens, or other appliances with digital clocks.
  - With this display, each of the 7 primary segments can be individually controlled, so there are  $2^7 = 128$  possible patterns.
  - Thus, it is possible to display any digit from 0 through 9, as shown below, and also certain letters.

 


Figure 1: 7-Segment Display, Hexadecimal

## Project Creation

2. Download `lab08a.vhd` and `lab08a.xdc` from Canvas and place them in a new folder titled `lab08a`.
3. Open Vivado and create a new project titled appropriately.
  - If you have not memorized how to do this by now, consult a previous lab handout (ex. [06B](#)).
  - For your convenience, the board identifier is `xc7a35tcpg236-1`.
    - You can copy and paste this directly into the search bar in the device select menu.
    - You can also find the board with the same options as before: `General Purpose`, `Artix-7`, `cpg236`, `-1`.

## Hardware Review and Upload

4. Open the file in the editor, and follow along with the instructor to review the hardware description.
  - To do this: inside the `Project Manager` pane, under the `Sources` subpane, and under the `Design Sources` folder, double-click the `lab08a.vhd` file.
5. Open `Elaborated Design`, review the schematic alongside the instructor, and **take screenshots for your report**.
6. Run synthesis and implementation and then generate the bitstream to program the device. Then, open the Hardware Manager.
  - **Take a screenshot of the resource utilization (LUTs and FFs) to add to your report.**
7. Before proceeding, plug the FPGA development board into your computer using the provided Micro-USB to USB-A cable.
8. At the top, in the green banner (or under the `Open Hardware Manager` dropdown) click `Open Target`, then `Auto Connect`.
9. Once the device is connected, select `Program Device` (in either of the locations where `Open Target` was previously).
  - See [06B-handout](#) for troubleshooting steps, or ask the instructor or TA.
10. Click `Program` to upload the bitstream to the FPGA.
  - When it is complete, you should see a pattern on the 7-segment display module on the FPGA development board.

# Hardware Testing and Analysis

11. At this time, **take a picture of the board** and the patterns on the 7-segment display module.
12. Does the **segment** output of the hardware description match the patterns you see on the four 7-segment displays on the board? Consult `lab08a.xdc` and the figures below for assistance.

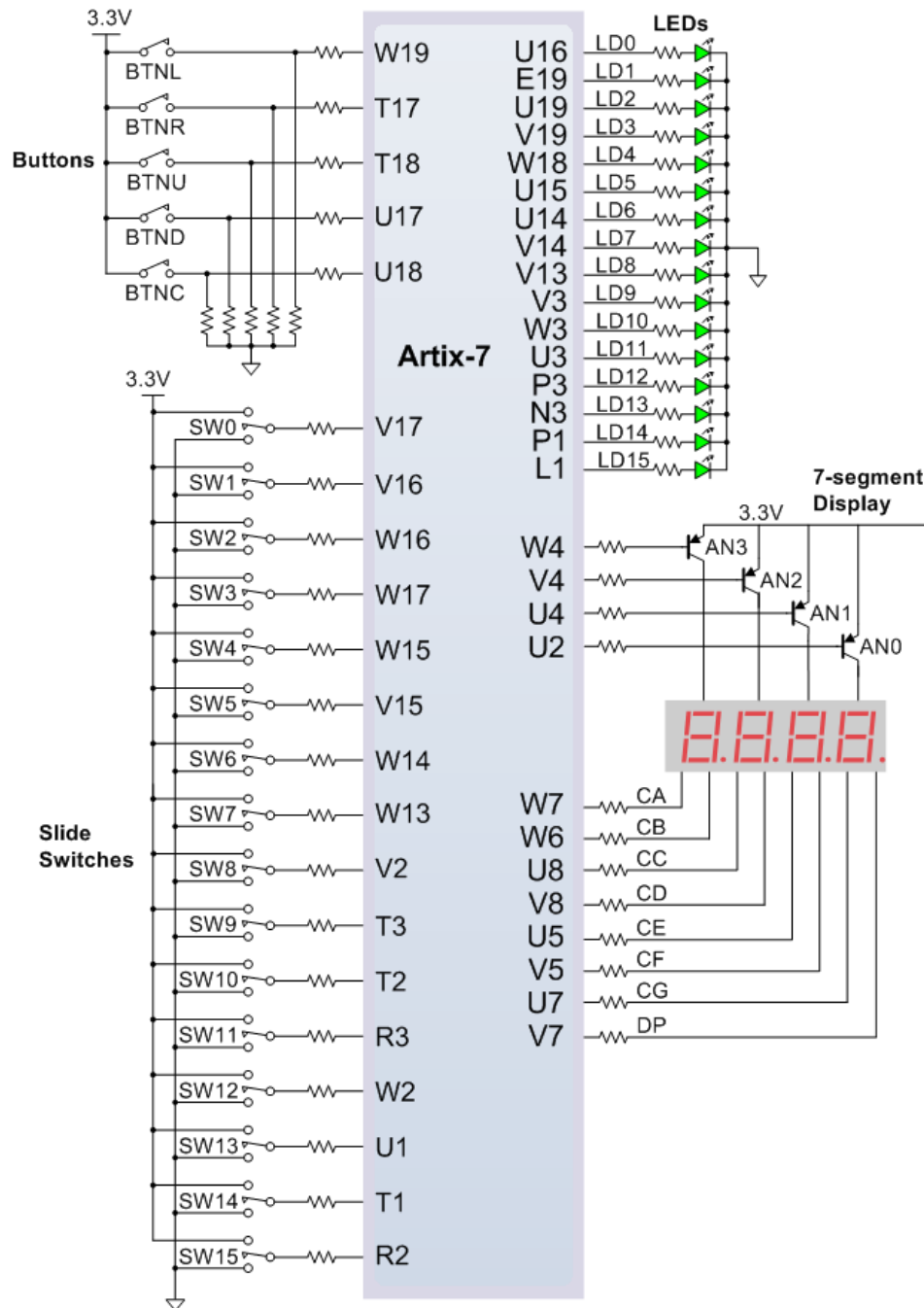


Figure 2: Basys 3 General Purpose Input-Output (GPIO) Diagram

 


Figure 3: Basys 3 Seven-Segment Display Diagram

13. Change the limit on the counter (`counter_limit`) from `2**18` ( $2^{18}$ ) to `2**10` ( $2^{10}$ ). Re-run the upload process (steps 6-10) and discuss with your lab group how the display output is affected. **Take a picture of the board.**
14. Change the limit to `2**26` ( $2^{26}$ ). Re-upload, **take a picture**, and discuss.
15. What is the optimal value of the limit, and why?

## Deliverables

- Include as part of your **informal report**:
  - A screenshot of the Elaborated Design schematic (Step 5)
  - A screenshot of the FPGA resource utilization (LUTs, FFs) (Step 6)
  - Pictures of the FPGA development board (Steps 11, 13, and 14)
  - Answers to handout questions (Steps 12, 13, 14, and 15)

## Outcomes

- Practice working with VHDL.
- Practice using Vivado for hardware synthesis and implementation.
- Practice programming and testing a hardware description on an FPGA development board.
- Understand how a seven-segment display functions.
- Understand the role of multiplexing in the seven-segment display module.