

ECCS1721-Homework#11

Problem 1

Using sequential (arbitrary) state assignment, realize the NRZ to Manchester code converter (described in lecture 27, slide 1) using D-Flip Flops.

Problem 2


Given the following state table:

Current state	Next state		output
	W=0	W=1	
A	B	C	1
B	D	F	1
C	F	E	0
D	B	G	1
E	F	C	0
F	E	D	0
G	F	G	0

1. Minimize the state table.
2. Using heuristic rules, assign the right values for the states in the minimized state table.
3. Implement the minimized state table using Toggle Flip Flops.

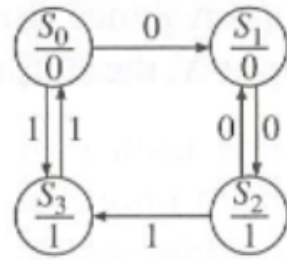1:

AB
 $S_0 = 00$
 $S_1 = 01$
 $S_2 = 10$
 $S_3 = 11$



(b) State graph

Present State	Next State		Present Output (Z)
	X=0	X=1	
S_0	S_1	S_3	0
S_1	S_2	—	0
S_2	S_1	S_3	1
S_3	—	S_0	1


(c) State table

$A^t B^t$	X = 0		X = 1		Z
	$A^{t+1} B^{t+1}$	$D_A D_B$	$A^{t+1} B^{t+1}$	$D_A D_B$	
00	01	01	11	11	0
01	10	10	---	---	0
10	01	01	11	11	1
11	---	---	00	00	1


$$D_A = \overline{B}X + B\overline{X}$$

$$D_B = \overline{B}$$

$$Z = A$$

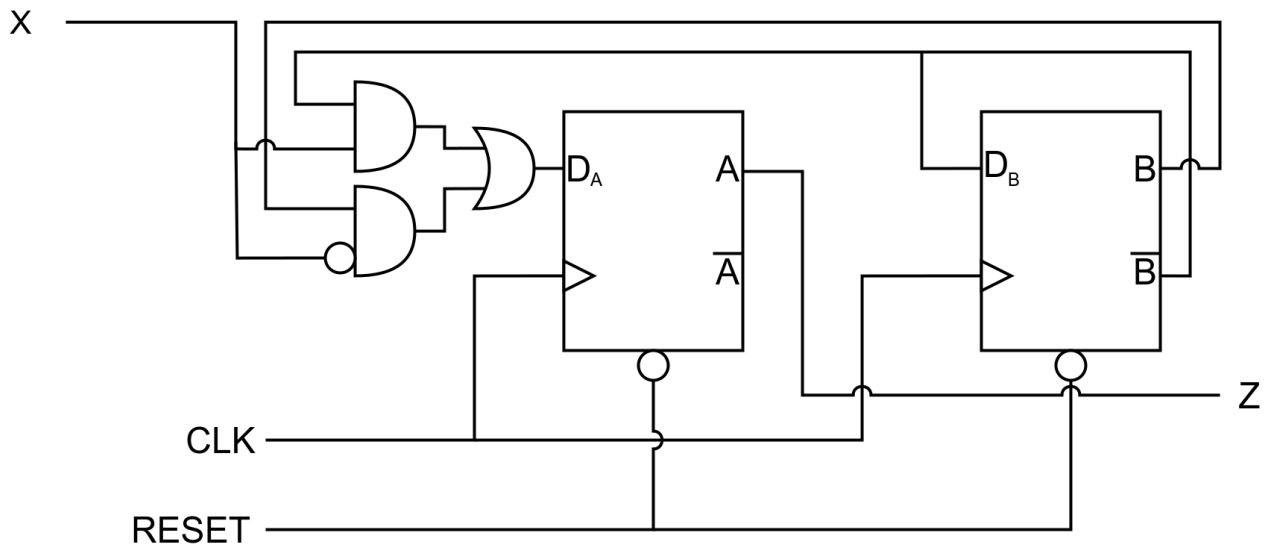

2.1:

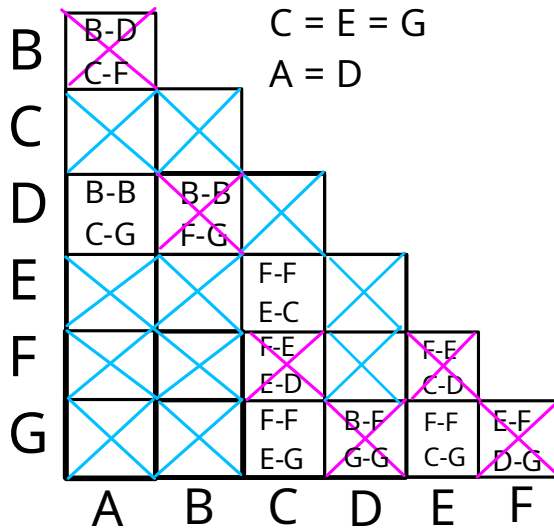

Current State	Next State		Output (Z)
	W = 0	W = 1	
A	B	C	1
B	A	F	1
C	F	C	0
F	C	A	0

2.2:

Rule 1: (A,C)

Rule 2: (B,C) (A,F) (F, C) (C, A)

Rule 3: (A,B) (C,F)

Q2 \ Q1	0	1
0	A	C
1	F	B

00 = A

01 = F

10 = C

11 = B

	$Q_2^t Q_1^t$	$Q_1^{t+1} Q_2^{t+1}$		Output (Z)
		W = 0	W = 1	
A:	00	11	10	1
C:	01	10	00	0
F:	10	01	10	0
B:	11	00	01	1

2.3:

$Q_2^t Q_1^t$	W = 0		W = 1		Output (Z)
	$Q_1^{t+1} Q_2^{t+1}$	$T_1 T_2$	$Q_1^{t+1} Q_2^{t+1}$	$T_1 T_2$	
00	11	11	10	10	1
01	10	11	00	01	0
10	01	11	10	00	0
11	00	11	01	10	1

$$T_1 = \overline{Q_1} \oplus Q_2 + \overline{W}$$

$$T_2 = \overline{Q_1} Q_2 + \overline{W}$$

$$Z = \overline{Q_1} \oplus Q_2$$

