

Question 1

Imagine a gear box created out of the different characters of your first name. For example instead of displaying N for neutral it displays F and instead of displaying R for reverse it displays I and son on. Write a truth table for the seven segment decoder used in this gear box. Your gear box should have the following inputs: P, N, R, and D. From the truth table write the Boolean expressions of the different decoder outputs. **Hint:** look at lecture 16 slide 5.

Question 2

The truth table of a 4 input priority encoder is as follows:

| I1 | I2 | I3 | I4 | O1 | O2 |
|----|----|----|----|----|----|
| 0 | 0 | 0 | 0 | X | X |
| 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 1 |
| 1 | 0 | 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 | 1 |

1. In few words, explain how the priority encoder works.
2. Using K-map find the simplified Boolean expression of O1 as sum of product.
3. Realize the expression in 2 using two input Nand/Not gates only and count the number of transistors.
4. Using K-map find the simplified Boolean expression of O2 as product of sum.
5. Realize the expression in 4 using Nor/Not gates only and count the number of transistors

A priority encoder outputs the position of the most significant bit of the input.

Question 3

1. Write the Boolean expression of an 8 to 1 multiplexer where S_2 , S_1 , and S_0 are used for the selection and D_0 to D_7 are the single bit inputs.
2. Write the Boolean expressions of a 1 to 8 demultiplexer where S_2 , S_1 , and S_0 are used for the selection and D_0 to D_7 are the single bit outputs.
3. Explain what need to be done to transform the above mux/demuxes to accept input/output signals of 8 bits each.

Increase the number of inputs or outputs to 8.


Question 4

In this problem please assume the select input as active high.

1. Continue the following truth table for a 2-to-1 multiplexer, where input1 and input2 are the two inputs to the multiplexer and Sel is the select.

| Input1 | Input2 | Sel | output |
|--------|--------|-----|--------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 |

2. Based on this truth table, draw the waveform of the output for the following input waveforms.

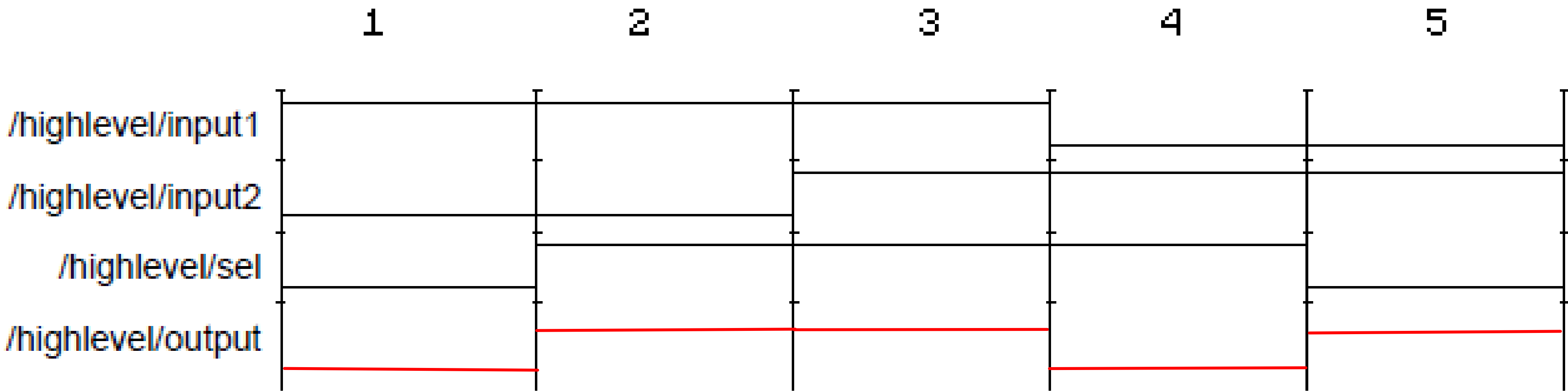

Question 5

Continue the truth table for a 1 to 4 demultiplexer:

| Input | Sel1 | Sel2 | Output1 | Output2 | Output3 | Output4 |
|-------|------|------|---------|---------|---------|---------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 1 |

Homework 5 active low

Q1)

| $I_3 I_2 I_1 I_0$ | A | B | C | D | E | F | G | |
|-------------------|---|---|---|---|---|---|---|---|
| 1 0 0 0 | 0 | 1 | 1 | 0 | 0 | 0 | 1 | C |
| 0 1 0 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | D |
| 0 0 1 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | R |
| 0 0 0 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | B |

$$A = 0$$

$$B = I_3$$


$$C = I_3$$

$$D = I_1$$

$$E = 0$$

$$F = 0$$

$$G = I_3 + I_2$$

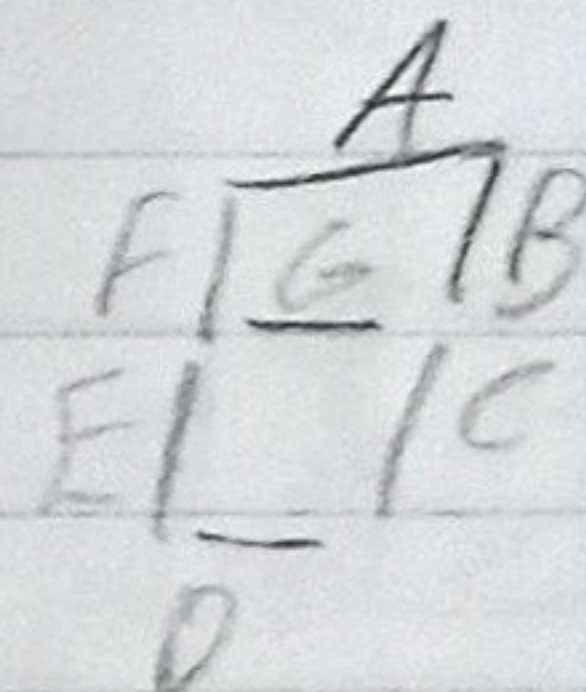


Q2
2)

| $I_3 I_2$ | $I_3 I_4$ | $I_3 I_4$ | $I_3 I_4$ | $I_3 I_4$ |
|-----------|-----------------------|-----------------|-----------------|-----------|
| 00 | $\bar{I}_3 \bar{I}_4$ | $\bar{I}_3 I_4$ | $I_3 \bar{I}_4$ | $I_3 I_4$ |
| 01 | 0 | 0 | 0 | 0 |
| 11 | 1 | 1 | 1 | 1 |
| 10 | 1 | 1 | 1 | 1 |

$$O_1 = I_1 + I_2$$

3)

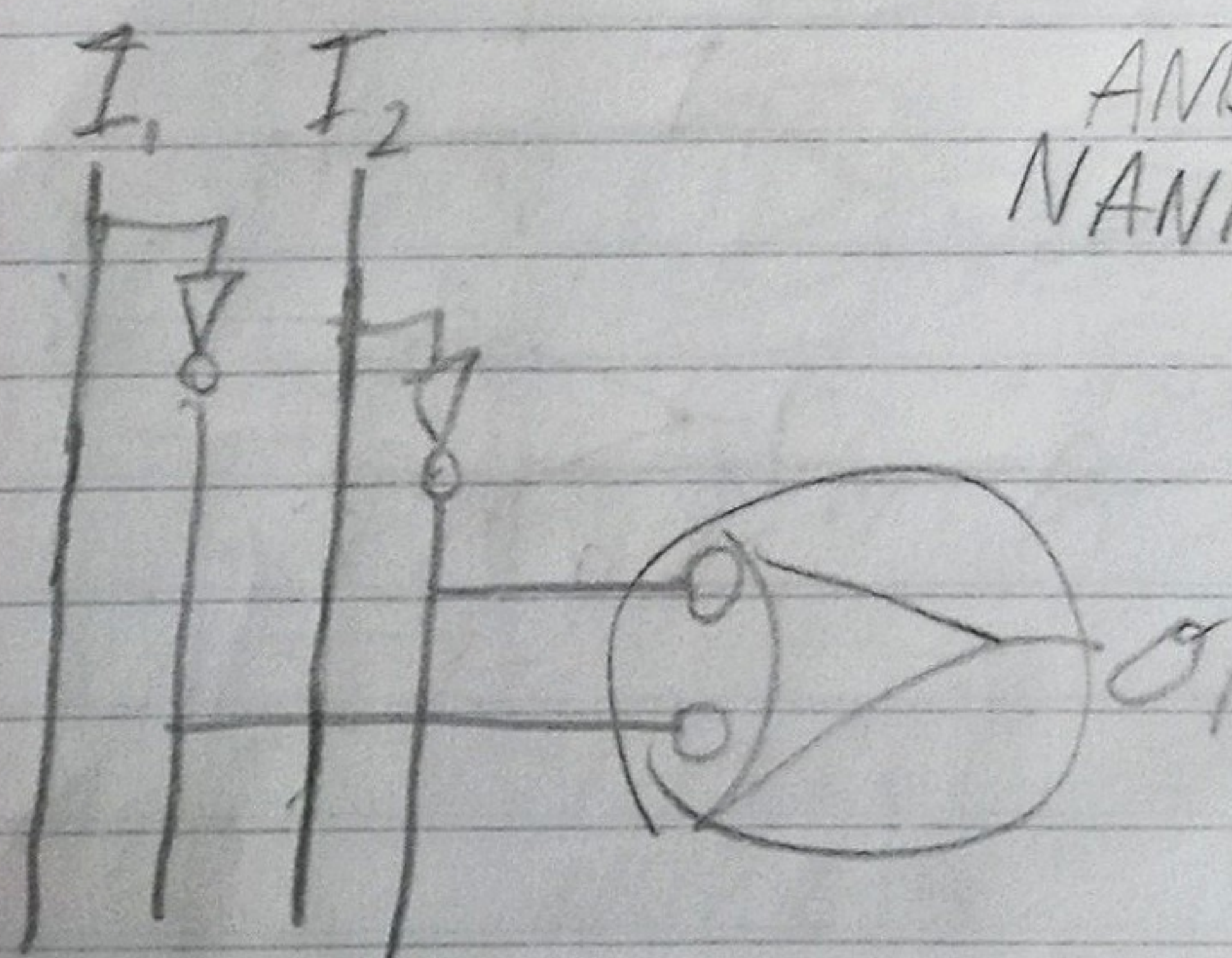

AND/OR = 6 Ts.
NAND/NOT = 4 Ts.

4)


| | $I_3 I_4$ | $\overline{I_3} I_4$ | $I_3 \overline{I_4}$ | $\overline{I_3} \overline{I_4}$ |
|---------------------------------|-----------|----------------------|----------------------|---------------------------------|
| $I_1 I_2$ | 1 | 1 | 1 | 1 |
| $\overline{I_1} I_2$ | 0 | 0 | 0 | 0 |
| $I_1 \overline{I_2}$ | 1 | 1 | 1 | 1 |
| $\overline{I_1} \overline{I_2}$ | 1 | 1 | 1 | 1 |

$$\overline{Y} = \overline{I_3} \overline{I_1} + \overline{I_1} I_2$$

$$Y = (I_3 + I_1)(I_1 + \overline{I_2})$$

5) I_1, I_2, I_3, I_4

AND/OR = 1875.
NOR/NOT = 1275.

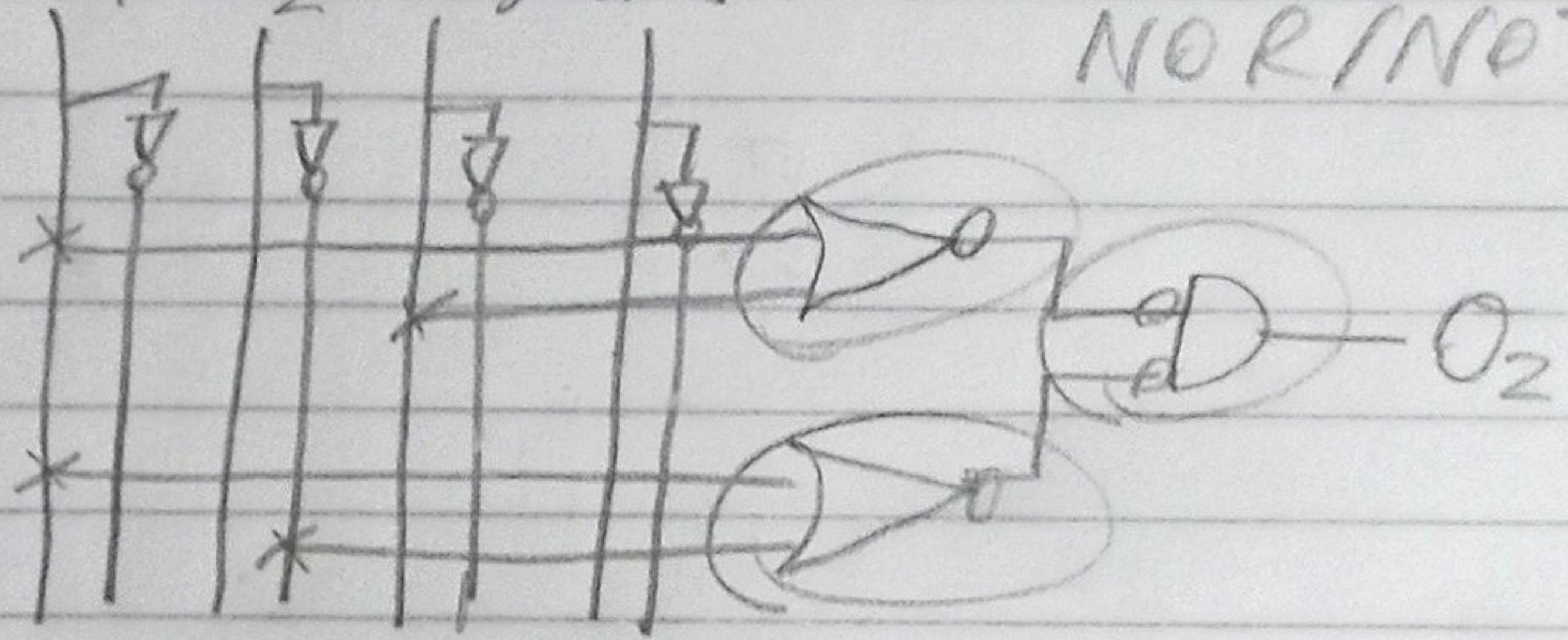

Q3

1) $D_0 = \overline{S_2} \overline{S_1} \overline{S_0} I_0 + \overline{S_2} \overline{S_1} \overline{S_0} I_1 + \overline{S_2} \overline{S_1} \overline{S_0} I_2 + \overline{S_2} \overline{S_1} \overline{S_0} I_3 + \overline{S_2} \overline{S_1} \overline{S_0} I_4 + \overline{S_2} \overline{S_1} \overline{S_0} I_5 + \overline{S_2} \overline{S_1} \overline{S_0} I_6 + \overline{S_2} \overline{S_1} \overline{S_0} I_7$

2)

$$D_0 = \overline{S_2} \overline{S_1} \overline{S_0} I$$

$$D_1 = \overline{S_2} \overline{S_1} S_0 I$$

$$D_2 = \overline{S_2} S_1 \overline{S_0} I$$

$$D_3 = \overline{S_2} S_1 S_0 I$$

$$D_4 = S_2 \overline{S_1} \overline{S_0} I$$

$$D_5 = S_2 \overline{S_1} S_0 I$$

$$D_6 = S_2 S_1 \overline{S_0} I$$

$$D_7 = S_2 S_1 S_0 I$$

3) Increase the number of inputs or outputs to 8.